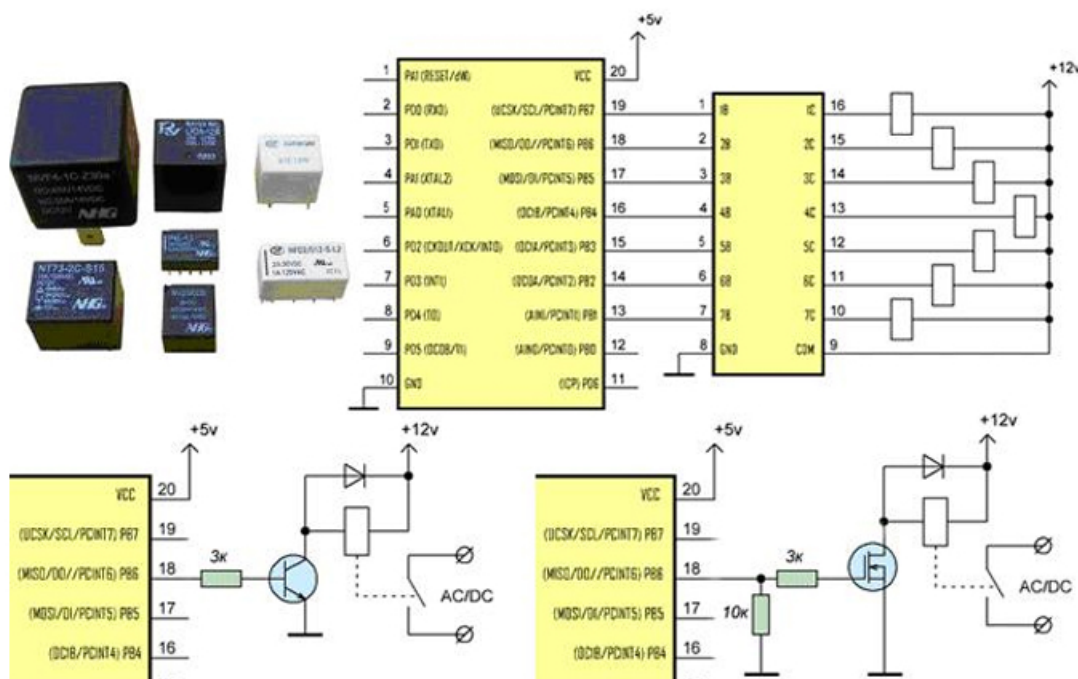
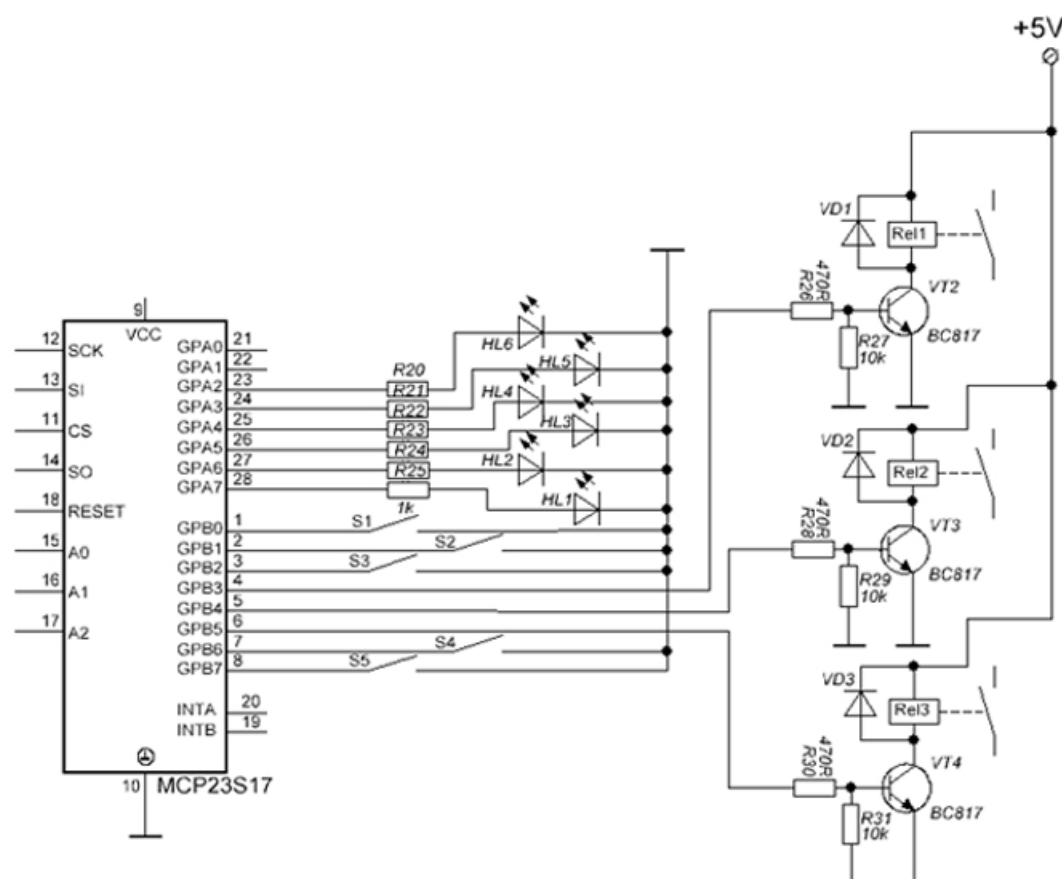


## Controlling power loads using relays

The most common ways of connecting relays to the microcontroller can be seen below:



Ways of connecting relays to the microcontroller



Connection diagram of the relay port expander connection